

# Unit 4: Boolean Algebra

CSE 220: System Fundamental I

Stony Brook University


Joydeep Mitra

# Digital Logic

- Digital systems perform operations on binary numbers.
- The fundamental building blocks used are *logic gates*.
- A logic gate is a digital circuit that takes *binary inputs* and produces *a binary output*.
  - Every logic gate is represented by a unique symbol
  - Inputs are drawn on the left (or top); outputs on the right (bottom)
  - Letters (e.g., A,B,C, and Y) indicate inputs and outputs
    - Letters may be subscripted with numbers (e.g.,  $A_0$ ,  $A_1$ )
- The relationship between inputs and output in a logic gate can also be represented in a *truth table*
  - A truth table indicates every combination of inputs and their corresponding output.
  - 1 indicates TRUE and 0 indicates FALSE
  - We will use 1, TRUE and 0, FALSE interchangeably
 
# NOT Gate


- Has one input and one output.
- If input is TRUE, output is FALSE and vice-versa.
- The NOT gate is also called an inverter.



- The line over  $A$  should be read as "NOT  $A$ "
- An alternative notation is  $A'$  also read as "NOT  $A$ "
 
# Buffer


- Has one input and one output.
- If input is TRUE, output is TRUE and vice-versa.
- The buffer is like a wire; output is same as input.
- From digital perspective a buffer might seem useless.
- But, from an analog perspective, it has numerous desirable characteristics (e.g., add delay).



$A$	$Y$
0	0
1	1
 
# AND Gate

- Two-input gate.
- Output is TRUE *if and only if* both inputs are TRUE; FALSE otherwise.
- Typical notation is  $Y = AB$ , other notations are used such as  $Y = A \cdot B$  or  $Y = A \cap B$




	<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1

- By convention, input combinations in truth table are listed as **00,01,10,11**
 
# OR Gate


- Two-input gate
- OR Gate output is TRUE if either of the inputs (or both) are TRUE; otherwise, FALSE
- Typical notation is  $Y = A+B$ , read as “Y equals A or B”
- Other notations include  $Y = A \cup B$ , read as “Y equals A union B”



<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	1
1	1	1

 
# NAND/NOR Gate

- A gate can be inverted by adding a bubble before the gate
- NAND gate is *inverted AND*
  - Output is FALSE *if and only if* both inputs are TRUE; otherwise, FALSE
- NOR gate is *inverted OR*
  - Output is TRUE *if and only if* both inputs are FALSE; otherwise, TRUE



$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


$$Y = \overline{A+B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0
 
# XOR Gate

- Two-input gate
- Output is TRUE if and only if either inputs are TRUE (not both); otherwise, FALSE




$A$	$B$	$Y$
0	0	0
0	1	1
1	0	1
1	1	0

- An N-input XOR gate can be used to check even/odd parity; TRUE for odd no. of inputs.


 
# XNOR Gate

- Inverted XOR
- Output is TRUE if and only if inputs are the same; otherwise, FALSE




<i>A</i>	<i>B</i>	<i>Y</i>
0	0	1
0	1	0
1	0	0
1	1	1

# Multiple Input Gates

- Many Boolean function (or gates) work with 3 or more inputs
- Common ones include AND, OR, XOR, NAND, NOR, and XNOR
- E.g., N-input AND produces TRUE when *all* inputs are TRUE
- E.g., N-input OR produces TRUE when *at least one* input is TRUE
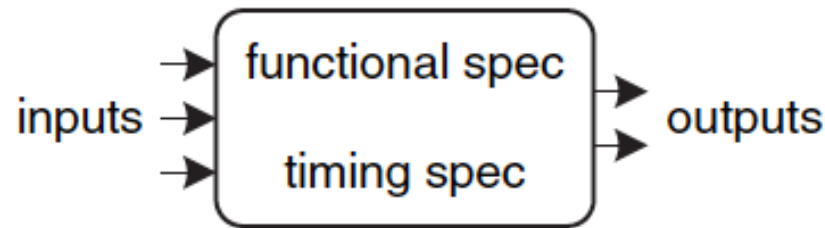
# Combinational Circuit Design


- A circuit is a network that processes *discrete-valued* variables
- You can view a circuit as a *black box* with the following elements:
  - *Input terminals*
  - *Output terminals*
  - A *functional specification* to define the relationship between inputs and outputs
  - A *timing specification* to define the delay between inputs changing and outputs responding



- A circuit can be
  - combinational – output is a function of input
  - sequential – output is a function of input and memory. More later.
 
# Peering Into The Black Box

- The black box has
  - Elements – circuits with inputs, outputs, and specifications
  - Nodes – wire to convey *voltage* that indicates discrete-valued variable
  - Nodes are *input*, *output*, or internal



- The illustration has 3 elements – E1, E2, and E3
- Nodes A,B,C are inputs
- Nodes Y,Z are outputs
- n1 is an internal node

# Specification vs Implementation


- Specification indicates "what" is the circuit
- Implementation indicates "how" the circuit will be built




$$Y = F(A, B) = A + B$$

**Specification**

(CL indicates combinational circuit)

 

**Implementation 1**

 


**Implementation 2**

# Rules of Combinational Composition

- In general, a circuit is combinational if
  - It is made of interconnected circuit elements
  - Every circuit is combinational
  - Every node is an input terminal, output terminal, or connected to the output terminal of an element
  - circuit has no cycles
 
# Specification vs Implementation

- Consider another example – *full adder*
- The equations specify the function of outputs in terms of inputs



$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

- More about implementation later

# Boolean Equation

- Boolean equation involve variables that are either TRUE or FALSE
- They can be used to describe the relationship between inputs and outputs
- But, first let's define a few terms



# Terminology

- **Complement:** variable with a bar over it or a tick mark:
  - $A', B', C'$
- **Literal:** an *instance* of a variable or its complement present in an expression
  - $A, A', B, B', C, C'$
- **Product** of literals:  $AB'C$
- **Sum** of literals:  $A + B' + C$
- **Minterm:** a product that includes *all* input variables
  - For a 3-input circuit (inputs:  $A, B, C$ ),  $AB'C$ ,  $A'BC'$  and  $ABC$  would be minterms, but  $AB'$  and  $BC$  would not be minterms
- **Maxterm:** a sum that includes *all* input variables
  - For a 3-input circuit,  $A + B' + C$  and  $A' + B + C'$  would be maxterms, but  $A + B'$  and  $B + C$  would not be maxterms

# Sum-of-Products Form

- A truth table has  $2^N$  rows for  $N$  inputs, one for each combination of inputs
- Each row is associated with a **minterm that is TRUE** for the row
- Minterms are numbered starting with 0
  - Minterm 0 is  $m_0$ , minterm 1 is  $m_1$ , and so on ...

$A$	$B$	$Y$	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	$m_0$
0	1	1	$\bar{A} B$	$m_1$
1	0	0	$A \bar{B}$	$m_2$
1	1	0	$A B$	$m_3$

- A Boolean equation can be represented as the **sum of minterms that have output 1 or TRUE**
  - $Y = A' B$

# Sum-of-Products Form

- This *sum of minterms* equation is called the **sum-of-products** form or **SOP** form.
- It is the sum (OR) of products (ANDs forming minterms).
- Generally, for the sake of consistency, if there is more than one minterm with output 1, we write them in order that they appear in the truth table.

<i>A</i>	<i>B</i>	<i>Y</i>	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	$m_0$
0	1	1	$\bar{A} B$	$m_1$
1	0	0	$A \bar{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = A' B + AB$$

Notice the equation has **4 literals**

# Sum-of-Products Form

- SOP form can also be written in **sigma notation**
- For example,  $Y = A'B + AB$  could also be written  $F(A, B) = \Sigma(m_1, m_3)$  or  $F(A, B) = \Sigma(1, 3)$  or  $F(A, B) = \Sigma m(1, 3)$
- Note that you MUST list the input variables in the same order as the truth table: start with 0 and increment the count from there

# Product-of-Sums Form

- Product-of-sum or **POS** is an alternative way to express Boolean equations
- Each row in the truth table corresponds to a **maxterm that is FALSE** for that row
- Boolean equation is expressed as the **product of maxterms with output FALSE or 0**

<i>A</i>	<i>B</i>	<i>Y</i>	maxterm	maxterm name
0	0	0	$A + B$	$M_0$
0	1	1	$A + \overline{B}$	$M_1$
1	0	0	$\overline{A} + B$	$M_2$
1	1	1	$\overline{A} + \overline{B}$	$M_3$

$$Y = (A + B) (A' + B)$$


- SOP and POS are equivalent. Why?
  - **De Morgan's Law**
  - More on that shortly!

# Product-of-Sums Form

- POS form can also be written in **pi notation**
- For example,  $Y = (A + B)(A' + B)$  could also be written as  $F(A, B) = \Pi(M_0, M_2)$  or  $F(A, B) = \Pi(0, 2)$  or  $F(A, B) = \Pi M(0, 2)$
 
# Example: DivBy4

- Consider designing a circuit that returns TRUE if a 3-bit number is divisible by 4 and FALSE otherwise
- Write a Boolean equation in **SOP** form and draw its circuit diagram
- $\Sigma(m_0, m_4) = A'B'C' + AB'C'$ 
  - The formula has 6 literals




A	B	C	$F(A, B, C)$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

# Example: DivBy4

- Write a Boolean equation in **POS** form and draw its circuit diagram

- $\Pi(M_1, M_2, M_3, M_5, M_6, M_7)$
 
$$= (A + B + C')(A + B' + C)(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C')$$



A	B	C	$F(A, B, C)$
0	0	0	1'
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0



# SOP vs POS

- They are **duals** of each other; equivalent ways of expressing the same function
- Generally, we use SOP if the truth table contains fewer 1s in output than 0s
- Similarly, we use POS if the truth table contains fewer 0s in output than 1s
- SOP and POS are called *two-level logic* because they use two gate levels : AND-OR or OR-AND
- A term is the minimal unit of a Boolean expression
- A term denotes the first-level gate from the perspective of a circuit
  - $ABC$  has one term, but  $AB + BC$  has two terms
  - Likewise,  $(A+B+C)$  has one term but  $(A+C)(A+B'+C)$  has two terms

# Minterm vs Maxterm

- A Boolean equation is *satisfiable* if at least one combination of inputs makes the output TRUE.
- SOP needs at least one term to make the equation *satisfiable*. Hence, its terms are called *minterms*
- POS needs all terms to make the equation *satisfiable*. Hence, its terms are *maxterms*.

# Boolean Algebra

- So far, we have used truth tables to create Boolean expressions (SOP and POS)
- But such expressions may not lead to the simplest set of logic gates
- Boolean Algebra provides axioms and laws/theorems to simplify Boolean equations
  - Axioms are like definitions assumed to be true.
  - Theorems are derived and proved using axioms.

# Axioms of Boolean Algebra

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\bar{0} = 1$	A2'	$\bar{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

- There are 5 axioms and their duals
- Axioms A1 and A1' indicate that we are in a *binary field*, i.e., Boolean variable B is 0 when its not 1 and vice-versa
- Axioms A2 and A2' indicate the NOT gate
- Axioms A3-A5 denote the AND gate
- Axioms A3' -A5' denote the OR gate

# One Variable Theorems

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

- **Identity.** The result of (any variable)  $B$  AND  $1$  is always  $B$ ; its dual states that  $B$  OR  $0$  is always  $B$
- **Null Element.** The result of ANDing any variable with  $0$  is always  $0$ ; its dual, ORing anything with  $1$  is always  $1$
- **Idempotency.** AND/ORing a variable  $B$  with itself gives back variable  $B$
- **Involution.** Complementing a variable twice gives back the same variable
- **Complement.** A variable AND its complement results in  $0$ ; its dual OR results in  $1$


# Several Variable Theorems

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + (B \bullet D) = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem

- **Commutativity.** Like in algebra the order of the variables does not matter.
- **Associativity.** The variable groupings do not matter. Same as algebra.
- **Distributivity.** T8 shows that AND distributes over OR and its dual shows that OR distributes over AND. Notice T8' is not allowed in algebra.
- **Covering, Combining, and Consensus** are used to eliminate redundant variables.
 
# De Morgan's Theorem

- De Morgan's Theorem is a significant result (named after Augustus De Morgan).
- From De Morgan, we can infer that:
  - A NAND gate is equivalent to an OR gate with inverted inputs!
  - A NOR gate is equivalent to an AND gate with inverted inputs!



# De Morgan's Theorem

- De Morgan's shows that SOP and POS are equivalent
- Consider the truth table:

$A$	$B$	$Y$	$\bar{Y}$	minterm
0	0	0	1	$\bar{A} \bar{B}$
0	1	0	1	$\bar{A} B$
1	0	1	0	$A \bar{B}$
1	1	1	0	$A B$

$$Y' = A' B' + A' B$$

From involution,  $Y'' = Y$

$$\text{Hence, } Y'' = (A' B' + A' B)'$$

$$\Rightarrow (A' B')' \cdot (A' B)'$$

$$\Rightarrow (A+B) \cdot (A+B')$$

} De Morgan's



# Simplifying Equations – Prime Implicant Rule

- Given a Boolean equation in SOP, look for the form  $\mathbb{P}A + \mathbb{P}A'$  and then combine them;  $\mathbb{P}$  is any **implicant**
- The idea is to obtain a **minimized equation** with *fewest possible implicants*
- If several *minimized* equations exists, pick the one with the fewest no. of literals
- A **prime implicant** is one which cannot be combined with other implicants to create a new implicant with fewer literals
- The implicants in a *minimal* equation are *prime implicants*.

# Simplifying Equations – Prime Implicant Rule

Step	Equation	Justification
	$\overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$	
1	$\overline{B}\overline{C}(\overline{A} + A) + A\overline{B}C$	T8: Distributivity
2	$\overline{B}\overline{C}(1) + A\overline{B}C$	T5: Complements
3	$\overline{B}\overline{C} + A\overline{B}C$	T1: Identity

- Notice that the pair of terms  $A'B'C' + AB'C'$  has the form  $PA + PA'$
- We combine them to get  $B'C'$
- We now have  $B'C' + AB'C$ ; both terms are prime implicants so further simplification by combining implicants is not possible!
- But we can further simplify using Boolean Algebra theorems

$$\begin{aligned}
 & B'C' + AB'C \\
 &= B'(C' + AC) && \text{(Distributivity)} \\
 &= B'(C' + A)(C' + C) && \text{(Distributivity)} \\
 &= B'(C' + A)(1) && \text{(Identity)} \\
 &= B'(C' + A)
 \end{aligned}$$

# Simplifying Equations – Duplicating Term Rule

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	T3: Idempotency
2	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B}(\overline{C} + C)$	T8: Distributivity
3	$\overline{B} \overline{C}(1) + A \overline{B}(1)$	T5: Complements
4	$\overline{B} \overline{C} + A \overline{B}$	T1: Identity

- But we can also pair  $\mathbf{AB'C'}$  +  $\mathbf{AB'C}$  ?
- We can combine them to get  $AB'$
- Further, implicants  $B'C'$  and  $AB'$  share the minterm  $AB'C'$
- When implicants share a minterm, the minterm can be **duplicated** for more simplification
- Thus,  $A'B'C' + \mathbf{AB'C'} + AB'C = A'B'C' + \mathbf{AB'C'} + \mathbf{AB'C'} + AB'C$
- Suddenly we have two instances of  $PA + PA'$ !
- For each, we use the previous method of combination to get  $B'C' + AB'$
- Simplify further by Distributivity to gets fewer literals  $B'(A + C')$

# Simplifying Equations – Expand Term Rule

- Sometimes it helps to expand an equation to enable the implicant approach (e.g., turn  $AB$  into  $ABC + ABC'$ )
  - This works! But why? recall *identity* and *complement*.

- Example:

$$AB + A'C + BC$$

$$\Rightarrow AB + A'C + ABC + A'BC$$

*Distributivity*

$$\Rightarrow AB(1+C) + A'C(1+B)$$

*Distributivity*

$$\Rightarrow AB + A'C$$

*Null Element*

# Simplifying Equations

- Let's try another example
- Show that  $Y = A'BC + (BC')' + BC$  can be simplified to  $Y = B' + C$

$$A'BC + (BC')' + BC$$

$$\Rightarrow BC(A' + 1) + (BC')'$$

$$\Rightarrow BC + (BC')'$$

$$\Rightarrow BC + B' + C$$

$$\Rightarrow B' + C(B + 1)$$

$$\Rightarrow B' + C$$

*Distributivity*

*Null Element*


*De Morgan's*

*Distributivity*

*Null Element*
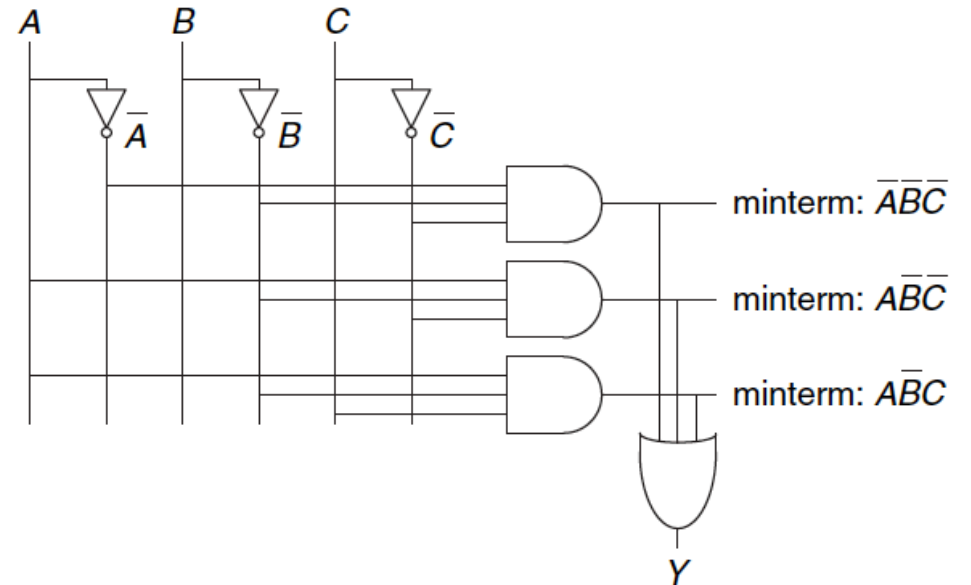
# From Logic to Gates


- Any Boolean equation can be represented as a *schematic*
  - A circuit diagram showing the elements and the wires that connect them
- Any SOP equation can be drawn systematically
  - Draw columns for inputs
  - Inverters in next column (if complement is necessary)
  - Draw AND gates for each minterm
  - Draw an OR gate that takes each output from the AND gates as inputs and has one output



$$Y = \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$$

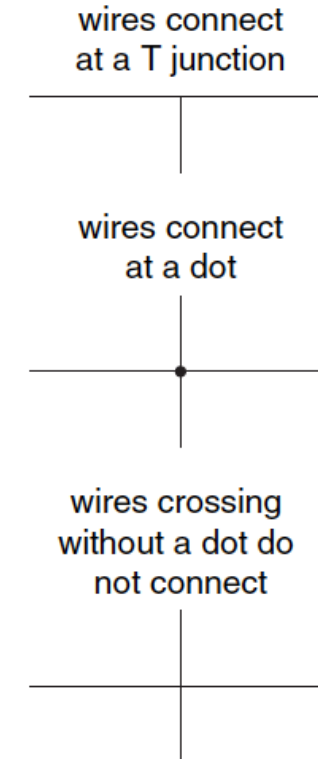
# From Logic to Gates

- When drawing circuits, we follow certain conventions for consistency
  - Inputs on the left (top) side of the schematic
  - Outputs on the right (bottom) side of the schematic
  - Generally, gates flow from left to right
  - Use straight wires
  - Wires always connect at a T junction
  - A dot where wires connect indicates a connection
  - Wires crossing without a dot indicates no connection



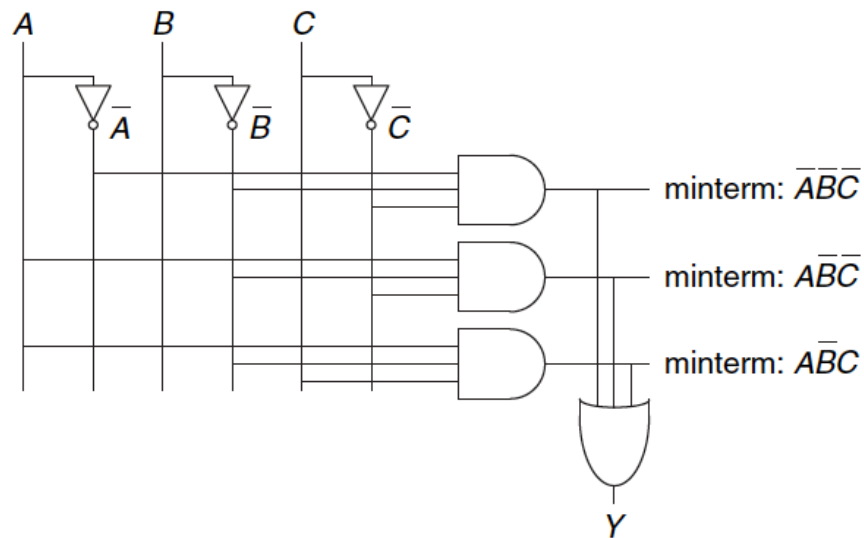
# From Logic to Gates

- Recall that  $A'B'C' + AB'C' + AB'C = B'C' + AB'$
- The simplified circuit will have less gates
  - Cheaper and faster!




VS.

 



 
# From Logic to Gates

- Can we do better?
  - Notice  $B'C'$  is an AND gate with inverted inputs (same as NOR)
  - We can remove 1 inverter!




vs.

 


$$B'C' + AB' = (B+C)' + AB'$$

# From Logic to Gates

- An alternative simplified circuit!

 

**vs.**

 


$$B'C' + AB' = B'(C' + A)$$

# Multiple Output Circuits

- Circuits may have more than one output (e.g., *priority circuit*)
- Assume a circuit with 4 inputs ( $A_3, A_2, A_1, A_0$ ) and 4 outputs ( $Y_3, Y_2, Y_1, Y_0$ )
  - $A_3$  has highest priority and  $A_0$  lowest
  - $Y_3$  is enabled when  $A_3$  is enabled
  - $Y_2$  is enabled when  $A_2$  is enabled but  $A_3$  is not
  - $Y_1$  is enabled when  $A_1$  is enabled but  $A_3$  and  $A_2$  are not
  - $Y_0$  is enabled when ONLY  $A_0$  is enabled
- We will write truth tables, Boolean equation, and sketch a circuit for this system
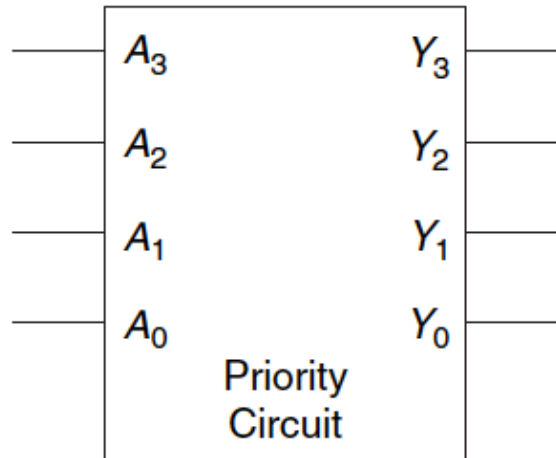
# 4-bit Priority Circuit

- Start with the truth table and the black box representation



$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

# 4-bit Priority Circuit

- Come up with Boolean equations.

$$Y_3 = A_3$$

$$Y_2 = A_3' A_2$$

$$Y_1 = A_3' A_2' A_1$$

$$Y_0 = A_3' A_2' A_1' A_0$$

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

# 4-bit Priority Circuit


- Design the circuit.

$$Y_3 = A_3$$

$$Y_2 = A_3' A_2$$

$$Y_1 = A_3' A_2' A_1$$

$$Y_0 = A_3' A_2' A_1' A_0$$

 




# 4-bit Priority Circuit

- Notice that if  $A_3$  is enabled then we don't care about other inputs.
- This notion can be used to shorten the truth table.
- Don't cares are represented as X in a truth table.
- X indicates the value can be 0 or 1.
- Later we will see how this can be used to simplify Boolean equations.

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0
   
# Electronic Die Example

- Let's design a circuit for an electronic die with the following specifications:
  - Inputs to the controller represent a 3-bit number ( $Q_2, Q_1, Q_0$ ), which indicates the number to be displayed
  - There are nine outputs,  $A - I$ , one for each of the dots
  - Based on the input no., the output dots will light up.
  - If the value 0 or 7 is given, no dots should light







# Electronic Die Example

- First step is to draw the truth table.

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

  

# Electronic Die Example

- Write the Boolean expression for each of the 9 outputs, using a minimal number of terms (SOP or POS)

- $$A = I$$

$$= (Q_2 + Q_1 + Q_0)(Q_2 + Q_1 + Q'_0)$$

$$(Q'_2 + Q'_1 + Q'_0)$$

$$= ((Q_2 + Q_1) + Q_0 Q'_0)(Q'_2 + Q'_1 + Q'_0)$$

$$= (Q_2 + Q_1)(Q'_2 + Q'_1 + Q'_0)$$

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

# Electronic Die Example

- Write the Boolean expression for each of the 9 outputs, using a minimal number of terms (SOP or POS)
- $B = H = 0$

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

# Electronic Die Example

- Write the Boolean expression for each of the 9 outputs, using a minimal number of terms (SOP or POS)
- $C = G = Q_2Q_1'Q_0' + Q_2Q_1'Q_0 + Q_2Q_1Q_0'$   
 $= Q_2Q_1' + Q_2Q_1Q_0'$

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

# Electronic Die Example

- Write the Boolean expression for each of the 9 outputs, using a minimal number of terms (SOP or POS)
- $D = F = Q_2Q_1Q_0'$

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

# Electronic Die Example

- Write the Boolean expression for each of the 9 outputs, using a minimal number of terms (SOP or POS)
- $E = Q_2'Q_1'Q_0 + Q_2'Q_1Q_0 + Q_2Q_1'Q_0$

$$= Q_2'Q_1'Q_0 + Q_2'Q_1Q_0 + Q_2Q_1'Q_0 + Q_2Q_1Q_0$$

$$= Q_2'Q_0 + Q_2Q_1'Q_0 + Q_2Q_1Q_0$$



$$= Q_2'Q_0 + Q_1Q_0$$

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

# Electronic Die Example

- Recall the electronic die problem.

$Q_2$	$Q_1$	$Q_0$	$A$	$B$	$C$	$D$	$E$	$F$	$G$	$H$	$I$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	1	0	1	1	0	1
1	1	1	0	0	0	0	0	0	0	0	0

  


# Electronic Die Example

- $A = I = (Q_2 + Q_1 + Q_0)(Q_2 + Q_1 + Q'_0)(Q'_2 + Q'_1 + Q'_0)$   
 $= ((Q_2 + Q_1) + Q_0 Q'_0)(Q'_2 + Q'_1 + Q'_0)$   
 $= (Q_2 + Q_1)(Q'_2 + Q'_1 + Q'_0)$
- $B = H = 0$
- $C = G = Q_2 Q'_1 Q'_0 + Q_2 Q'_1 Q_0 + Q_2 Q_1 Q'_0$   
 $= Q_2 Q'_1 + Q_2 Q_1 Q'_0$
- $D = F = Q_2 Q_1 Q'_0$
- $E = Q'_2 Q'_1 Q_0 + Q'_2 Q_1 Q_0 + Q_2 Q'_1 Q_0$   
 $= Q'_2 Q_0 + Q_2 Q'_1 Q_0$   
 $= Q'_2 Q_0 + Q_2 Q'_1 Q_0 + Q'_2 Q'_1 Q_0 = Q'_2 Q_0 + Q'_1 Q_0$




# Electronic Die Example

- Circuits in AND-OR or OR-AND Networks

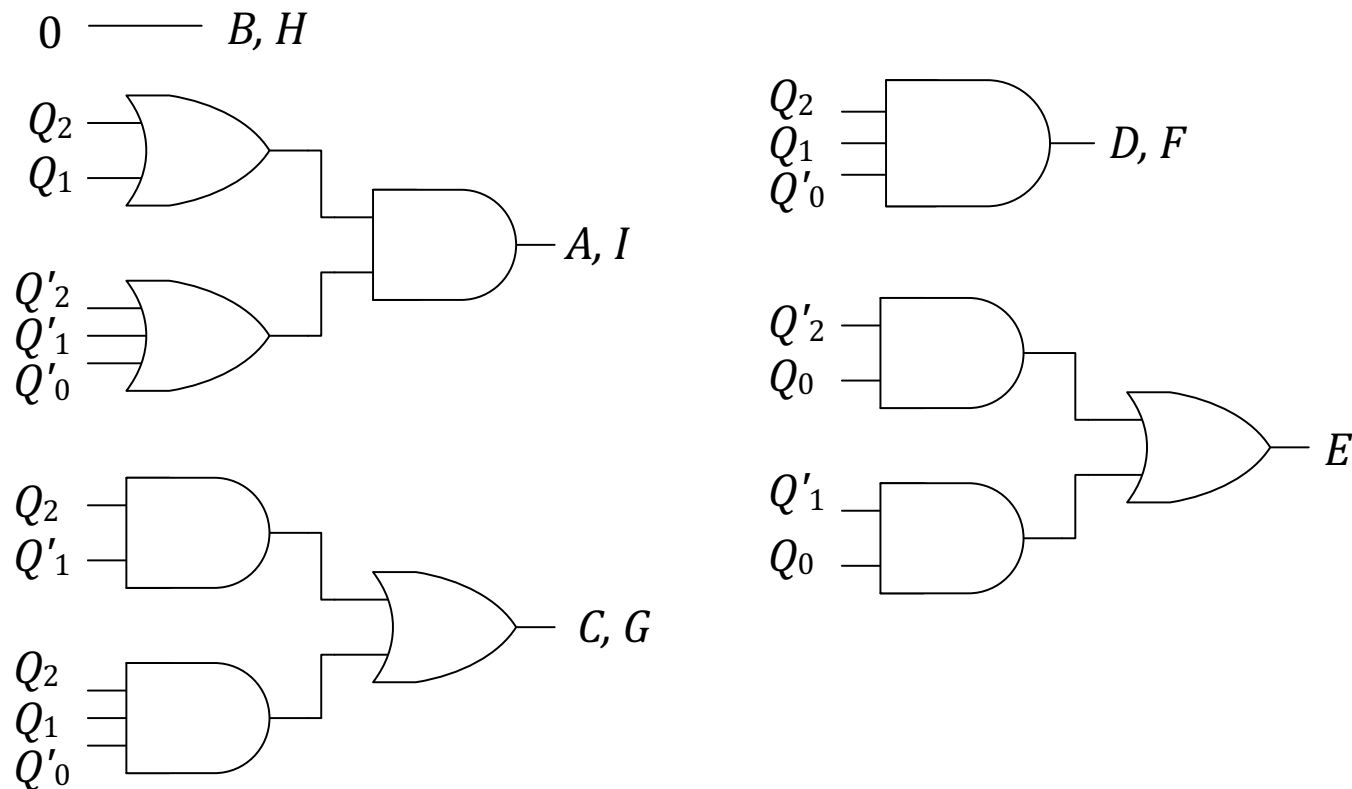

 
# Electronic Die Example

- Can you implement SOP in NAND-NAND and POS in NOR-NOR?
- Recall,  $Y'' = Y$  (involution) and DeMorgan's.
- Let's apply them to each output.
- $A = I = A'' = I'' = ((Q_2 + Q_1)(Q'_2 + Q'_1 + Q'_0))''$   
 $= ((Q_2 + Q_1)' + (Q'_2 + Q'_1 + Q'_0))'$



 
# Electronic Die Example

- $$C = G = C'' = G'' = (Q_2 Q'_1 + Q_2 Q_1 Q'_0)''$$
$$= ((Q_2 Q'_1)' \cdot (Q_2 Q_1 Q'_0)')'$$



 
# Electronic Die Example

- $D = F = D'' = F'' = (Q_2 Q_1 Q'_0)'' = (Q_2' + Q_1' + Q_0)'$



 - $E = E'' = (Q'_2 Q_0 + Q'_1 Q_0)'' = ((Q'_2 Q_0)' \cdot (Q'_1 Q_0)')'$



# Multiplier Example

- Let's design a black box with a decimal digit (0-9) encoded in 4-bit binary as input ( $A_3, A_2, A_1, A_0$ ).
- The output is the decimal digit multiplied by 3.
- The maximum possible output of the circuit is 27, so we need at least 5 bits for the output.
- We will draw a truth table first with 16 rows (4 inputs).
- But we don't care about value greater than 9!

A	3A
0	0
1	3
2	6
3	9
4	12
5	15
6	18
7	21
8	24
9	27

A3	A2	A1	A0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

X3	X2	X1	X0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	1
0	0	0	1
0	0	0	1
0	0	0	1
X	X	X	X
X	X	X	X
X	X	X	X
X	X	X	X
X	X	X	X

Y3	Y2	Y1	Y0
0	0	0	0
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0
1	1	1	1
0	0	1	0
0	1	0	1
1	0	0	0
1	0	1	1
X	X	X	X
X	X	X	X
X	X	X	X
X	X	X	X
X	X	X	X

# Multiplier Example

- Let's derive the equation for  $X_0$ .
- Recall X's are don't cares (considered 0 or 1 as per convenience.)

Let's consider all X's as 0.

$$\begin{aligned}
 X_0 &= A'_3 A_2 A_1 A'_0 + A'_3 A_2 A_1 A_0 + A_3 A'_2 A'_1 A'_0 + A_3 A'_2 A'_1 A_0 \\
 &= A'_3 A_2 A_1 (A_0 + A'_0) + A_3 A'_2 A'_1 (A'_0 + A_0) \\
 &= A'_3 A_2 A_1 A_0 + A_3 A'_2 A'_1
 \end{aligned}$$

A3	A2	A1	A0	X0
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

# Multiplier Example

- Let's consider all X's as 1 instead.
  - Create SOP with minterms.
  - Duplicate the minterm  $A_3A_2A_1A_0$
  - Apply the prime implicant rule to obtain
$$X_0 = A_3 + A_2A_1$$
- Considering X's as 1's helped us simplify the equation further!

A3	A2	A1	A0	X0
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1



# Multiplier Example

- Let's try another example.
- Derive the equation for  $X_1$ .
- Clearly  $X_1$  is all 0s.
- We must set all  $X$ 's to 0.
- We get  $X_1 = 0$ .

*Takeaway:*

- *It may be useful to have  $X$ 's in a truth table.*
- *$X$ 's can be 0 or 1.*
- *They are 0 or 1 if it helps us simplify further.*

A3	A2	A1	A0	X1
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X