

Unit 8: Multiplexers

CSE 220: System Fundamental I

Stony Brook University


Joydeep Mitra

Multiplexer Overview


- What is a multiplexer?
 - A multiplexer (also MUX) is a larger building block used to choose a data input from several data inputs based on one or more select/control signals
- Why use a multiplexer?
 - To build complex combinational circuits (an application of abstraction)
- Example: A 2:1 MUX with 2 data inputs, a select signal, and an output signal
 - The MUX chooses between D_0 and D_1 based on the select/control signal S

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Truth table of 2:1 MUX

 

Schematic of 2:1 MUX

 

Alternative schematic;
“MUX” label is optional


Edit: In lecture, I mistakenly say that 1 stands for select signal. The 1 stands for the output signal and not the select signal.

Implementing A Multiplexer

- A multiplexer can be easily implemented with sum-of-products logic


Y S		$D_{1:0}$			
		00	01	11	10
0	0	0	1	1	0
1	0	0	0	1	1

$$Y = D_0 \bar{S} + D_1 S$$

 


Wider Multiplexers

 - A 4:1 MUX has 4 data inputs, 2 control/select signals, and 1 output
- 4:1 MUX can also be implemented using SOP logic
- Similarly, 8:1 MUX will have 8 data inputs, 3 control signals, and 1 output
- In the same vein, 16:1 MUX will have 16 data inputs, 4 control signals, and 1 output
- In general, an N:1 MUX will have N data inputs, $\log_2 N$ control signals, and 1 output





Schematic of a 4:1 MUX

 

A 4:1 MUX implementation with SOP logic

Wider Multiplexers

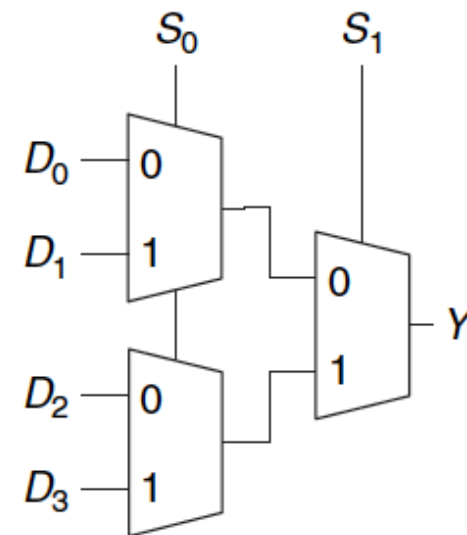 - A wider multiplexer can be implemented with narrower multiplexers. How?
 - Create a hierarchy of the available narrower MUXes
 - E.g., 4:1 MUX with two layers of three 2:1 MUXes
- Which is better for implementing MUX: narrower MUXes or SOP logic?
 - Depends on the target technology
 - Availability vs scalability tradeoffs are involved



Multiplexers As Minimal Complete Sets

- A **minimal complete set** is a set with the least number of unique gates that can be used to express any Boolean function
 - {AND, NOT}
 - {NAND} and {NOR}
 - {AND, NOT, OR} is complete but not minimal. Why?
 - For {AND, NOT}, OR is redundant; for {NOT, OR} AND is redundant
- *Multiplexers are a minimal complete set* as they can be used to express any Boolean function
- In general, a 2^N -input multiplexer can be programmed to perform any N-input logic function


Edit: In lecture, I mistakenly stated that NAND and NOR gates are not minimal complete sets. They are. You can express any Boolean function in terms NAND or NOR gates.

AND Gate With Multiplexer

- $Y(A, B) = AB$ is a logic function with 2 inputs
- We can implement this with a 4:1 MUX
 - A and B are control signals
 - 4 inputs mapped to either 0 or 1 based on Y's value in truth table
 - 0 is indicated by ground (triangle), and 1 is indicated by high voltage (flat bar)
- Can we do better?

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$Y = AB$

 


AND Gate With Multiplexer

- A MUX implementation of any logic function with N inputs can be cut into half by selecting one of the inputs to be the control signal
 - $2^N:1$ MUX becomes $2^{N-1}:1$
- General strategy:
 - Start with the truth table
 - Combine pairs of rows to eliminate the right-most input variable by expressing output in terms of this variable
- E.g., $Y(A, B) = AB$
 - When $A = 0$, $Y = 0$ regardless
 - When $A = 1$, $Y = 0$ if $B = 0$, and $Y = 1$ if $B = 1$
 - So, $Y = B$ when $A = 1$

$Y = AB$

A	B	Y	A	Y
0	0	0	0	0
0	1	0		
1	0	0	1	B
1	1	1		

 


XOR Gate With Multiplexer

- An XOR gate can be easily implemented using a 2:1 MUX

$Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


A	Y
0	B
1	\bar{B}

 

Example #1

- Implement the function $Y = AB' + B'C' + A'BC$. We only have 8:1 multiplexers


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 

Example #2

- Implement the function $Y = AB' + B'C' + A'BC$. We only have 4:1 multiplexers
- We reduce the truth table to 4 rows by basing the output on C

A	B	C	Y	A	B	Y
0	0	0	1	0	0	\bar{C}
0	0	1	0	0	1	C
0	1	0	0	1	0	1
0	1	1	1	1	1	0
1	0	0	1			
1	0	1	1			
1	1	0	0			
1	1	1	0			

 


Multiplexers From Boolean Equations

- In addition to the truth table approach, we can use Boolean algebra to design our circuits with muxes
- We need a Boolean equation in SOP form
- If not, then use Boolean algebra to re-write to SOP form (similar to K-maps)
- Key insight
 - An equation of the form $PA + P'B$ can be converted to a MUX where P is the selector/control variable, and A and B are the input signals
 - A and B may be the output of multiplexers as well

 Example #3

- Implement the function $F = ABC' + A'BC' + A'B'C' + BC$ using only 2:1 muxes
- Let's convert to SOP form
 - $$\begin{aligned} F &= ABC' + A'BC' + A'B'C' + BC \\ &= ABC' + A'BC' + A'B'C' + (A+A')BC \\ &= ABC' + A'BC' + A'B'C' + ABC + A'BC \end{aligned}$$
- We pick A as the control variable
 - $$\begin{aligned} F &= ABC' + A'BC' + A'B'C' + ABC + A'BC \\ &= A(BC' + BC) + A'(BC' + B'C' + BC) \\ &= A(B) + A'(C'1 + BC) \end{aligned}$$
- We will need two 2:1 muxes
 - With control variable A for main expression in F
 - With control variable C for the expression $(C'1 + BC)$



Example #4

- Let's try the same example with selector/control signal B

$$F = ABC' + A'BC' + A'B'C' + ABC + A'BC$$

$$= B(AC' + A'C' + AC + A'C) + A'B'C'$$


$$= B(C' + C) + B'(A'C')$$

$$= B(1) + B'A'C' + B'A0$$

$$= B(1) + B'(A'C' + A0)$$


- We will need two 2:1 muxes

 - With control variable B for main expression in F
- With control variable A for the expression $(A'C' + A0)$



 Example #5


- Implement the function $F = ABC' + A'BC' + A'B'C' + BC$ using only 4:1 muxes
- The SOP form
 - $F = ABC' + A'BC' + A'B'C' + ABC + A'BC$
- 4:1 MUX, so we need 2 control/selector variables. We pick AB
 - $$\begin{aligned} F &= ABC' + A'BC' + A'B'C' + ABC + A'BC \\ &= AB(C + C') + A'B(C' + C) + A'B'C \\ &= AB1 + A'B1 + A'B'C \\ &= AB1 + A'B1 + A'B'C' + AB'0 \end{aligned}$$



 Example #6

- Implement the function $F = ABC' + A'BC' + A'B'C' + BC$ using only 4:1 muxes
- The SOP form
 - $F = ABC' + A'BC' + A'B'C' + ABC + A'BC$
- 4:1 MUX, so we need 2 control/selector variables. We pick AC this time


$$\begin{aligned} F &= ABC' + A'BC' + A'B'C' + ABC + A'BC \\ &= AC'(B) + A'C'(B+B') + AC(B) + A'C(B) \\ &= AC'(B) + A'C'(1) + AC(B) + A'C(B) \end{aligned}$$



 Example #7

- Implement the function $F = ABC' + A'BC' + A'B'C' + BC$ using only 4:1 muxes
- The SOP form
 - $F = ABC' + A'BC' + A'B'C' + ABC + A'BC$
- 4:1 MUX, so we need 2 control/selector variables.
We pick BC this time

$$\begin{aligned} F &= ABC' + A'BC' + A'B'C' + ABC + A'BC \\ &= BC'(1) + B'C'(A') + BC(1) \\ &= BC'(1) + B'C'(A') + BC(1) + B'C(0) \end{aligned}$$



Points To Note

- Selecting different selector/control variables will result in different circuits
- The circuits may use different gates
- Which circuit to pick will ultimately depend on the target technology, the availability and cost of the gates involved
- As practice try implementing the following gates with MUXes
 - NOT
 - OR
 - NAND
 - NOR
 - XNOR