

Unit 11: Sequential Circuits

CSE 220: System Fundamentals I

Stony Brook University




Joydeep Mitra

Combination Vs Sequential

- In Combinational logic, outputs depend on current inputs
- In Sequential logic, outputs depend on current and prior inputs
- So, sequential logic has *memory*
- Sequential logic circuits remembers prior inputs in a set of bits called *state variables*; the set itself is called the *state*
- Outputs are a function of current inputs and state
- Sequential logic circuits are based on *bistable elements*

Bistable Element

- The fundamental building block of memory is the *bistable element*
 - Bistable because it has two *stable* states
- The element is designed as two inverters with two outputs, which are cross-coupled as inputs
- There are two cases to consider
 - **Q = 0**; input to I2 is 0 and output is Q', which is 1. Q' is input to I1, which outputs Q, which is 0. Our assumption Q = 0 is correct! Hence, *stable*.
 - **Q = 1**; input to I2 is 1 and output is Q', which is 0. Q' is input to I1, which outputs Q, which is 1. Our assumption Q = 1 is correct! Hence, *stable*.

   


Bistable Element

- A bistable element stores 1 bit. Why?
 - N stable states convey $\log_2 N$ bits of information
 - Bistable element has 2 stable states
- If $Q = 0$, then it will remain 0 forever
- If $Q = 1$, then it will remain 1 forever
- This notion of stability underlies the property of memory
- However, the initial state of a bistable element is unknown, differs each time circuit is turned on
- Hence, they cannot be practically used as the user cannot control the inputs to control state
- Consequently, we need bistable elements with inputs (latches and flip-flops)


SR Latch

 - The SR latch is composed of two cross-coupled NOR gates
- It has two inputs, S and R, and two outputs, Q and \bar{Q}
- Let's understand the circuit by exploring each input combination




The SR Latch

 - Case 1: $S = 0, R = 1$
- Then, $Q = 0, Q' = 1$




 - Case 2: $S = 1, R = 0$
- Then, $Q = 1, Q' = 0$



The SR Latch

 
- Case 3: $S = 1, R = 1$
- Then, $Q = 0, Q' = 0$




- So, when $S = R = 1$, both outputs are 0 (nonsense inputs!)

The SR Latch

 - Case 4A: $S = 0, R = 0, Q = 0$
- Then, $Q = 0, Q' = 1$



 - Case 4B: $S = 0, R = 0, Q = 1$
- Then, $Q = 1, Q' = 0$



Putting It Together

- Suppose Q has a known prior value (Q_{prev})
- When $S = 0$ and $R = 0$, circuit remembers Q_{prev}
- When $S = 1$, circuit “sets” Q to 1
- When $R = 1$, circuit “resets” Q to 0
- *The circuit has memory!*


S	R	Q	\bar{Q}
0	0	Q_{prev}	\bar{Q}_{prev}
0	1	0	1
1	0	1	0
1	1	0	0

Limitation Of SR Latch


- The S and the R inputs conflate the *what* and the *when*
- Specifically, asserting one of the inputs not only determines Q but also when Q should change!
- This is why we get nonsense outputs when both $S = 1$ and $R = 1$
- This is not a good design principle; the *what* and the *when* need to be separated
- **D latch** to the rescue! It has two inputs
 - A *data* input, D, controls what the next state should be
 - A *clock* input, CLK, controls when the state should change

D Latch

 - When $CLK = 0$, $S = 0$ and $R = 0$ (due to AND gate)
 - Hence, previous Q will be retained
- When $CLK = 1$, $S = D$ and $R = D'$
 - So, if D is set to 1, Q is set to 1
 - If D is reset to 0, Q is reset to 0



Circuit

 

Symbol

Putting It Together

- The Clock controls when data flows through the latch
- When $CLK = 1$, latch is *transparent*, i.e., allows new data
- When $CLK = 0$, latch is *opaque*, i.e., blocks new data and retains old data
- A D latch is also called a *level-sensitive* latch



CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X	\overline{X}	0	0	Q_{prev}	\overline{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0
...						

Limitation of D Latch

- Notice when $CLK = 1$, Q changes state
- If CLK stays at 1, then Q will keep changing, making the circuit unstable
- The **D flip-flop** addresses this by changing state at a particular *instant* in time

D Flip-Flop


- A D flip-flop can be built from two back-to-back D latches, controlled by complementary clocks
- When $CLK = 0$, latch L1 is transparent and L2 is opaque
 - The value at D propagates to Q via N1
- When $CLK = 1$, latch L1 is opaque and L2 is transparent
 - The value at D is blocked from reaching Q
- When clock rises from 0 to 1, value at D is copied to Q
- At all other times, Q retains its old value
- A D flip-flop is also called an *edge-triggered* or a *positive edge-triggered* flip-flop

 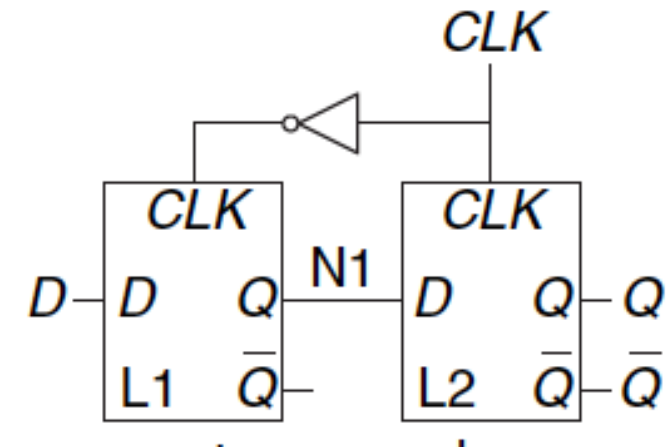

D flip-flop symbols

Register

 
- An N-bit register is a bank of N flip-flops with a common CLK to update all N bits at the same time




4-bit register schematic and symbol

Enable Flip-Flop

- Recall the D flip-flop changes state when clock edge rises from 0 to 1
- But we may not want to update state at every rising clock edge
- An *Enabled flip-flop* allows us to update state at every alternate rising edge of the clock
- To this end, it add a 2:1 MUX to the D flip-flop
 - with **EN** as select signal
 - **D** and **Q_{prev}** as inputs signals
- When **EN** = **0**, the clock is ignored old value is retained
- When **EN** = **1**, behaves like D flip-flop

 


Schematic

 

Symbol


Timing of Sequential Circuits

 - Recall that a digital clock is represented as a timing waveform with rising edges indicating the transition from 0 to 1
- To appreciate the differences between latches and flip-flops, consider the timing waveform below
- Using the waveform, we will determine the output, Q , for each device
 - We assume a slight delay for Q to respond to input changes



Timing of Sequential Circuits

 
- Initial value of Q is 0 or 1 (indicated by the horizontal line pair)
- For the latch
 - on the rising edge of CLK, $D = 0$, so $Q = 0$
 - Subsequently, Q follows D whenever CLK = 1, otherwise Q is retained
- For the flip-flop,
 - On the rising edge of CLK, D is copied to Q
 - At all other times, Q is retained



Timing Waveforms: Example #1

S	R	Q	\bar{Q}
0	0	Q_{prev}	\bar{Q}_{prev}
0	1	0	1
1	0	1	0
1	1	0	0

 - Consider the input waveform below of an SR latch. Sketch the output (Q) of the latch.




- Answer:

Timing Waveforms: Example #2

S	R	Q	\bar{Q}
0	0	Q_{prev}	\bar{Q}_{prev}
0	1	0	1
1	0	1	0
1	1	0	0

 
- Consider the input waveform below of an SR latch. Sketch the outputs (Q and Q') of the latch.



- Answer:

Timing Waveforms: Example #3

 
- Consider the input waveform below of a D latch. Sketch the output (Q) of the latch.



- Answer:

Timing Waveforms: Example #4

 - Consider the input waveform below of a D flip-flop. Sketch the output (Q) of the flip-flop.




- Answer:

Timing Of Sequential Logic

- Recall that a flip-flop copies input D to output Q on the rising edge of the clock.
- What happens if D is changing the same time the clock rises?
 - We cannot take its input
 - The clock period (T_c) has to be long enough for D to be stable before we can take its input (also called sampling)
- This limitation restricts the system speed


Timing Of Sequential Logic

- Sequential circuits have timing specifications to reason about the delay caused by changing signals
 - setup time:** denoted t_{setup} , this is the length of time *before* the clock edge that input data must be stable for a circuit to *sample* the input correctly
 - hold time:** denoted t_{hold} , this is the length of time *after* the clock edge that input data must be stable for the circuit to *sample* the input correctly
 - aperture time:** $t_{setup} + t_{hold}$

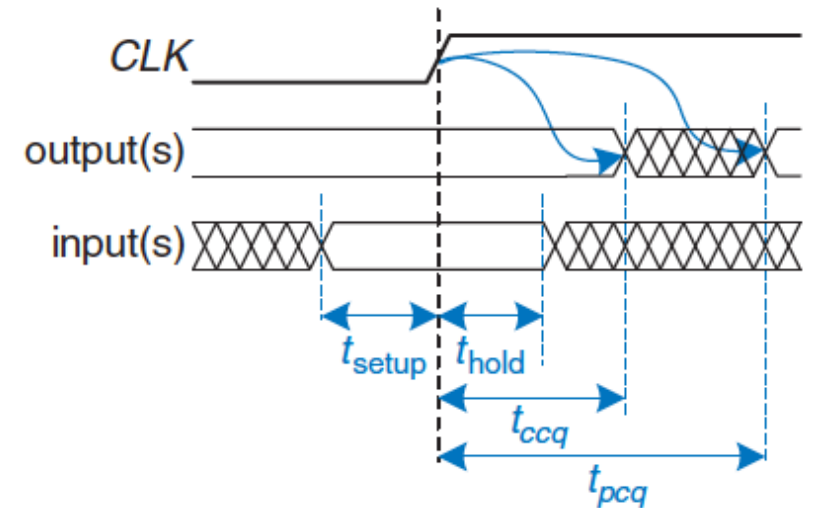

Timing Of Sequential Logic

- Additional Specifications
 - **clock-to-Q contamination delay:**
denoted t_{ccq} , this is the minimum length of time after the clock edge that we will expect to see changes in the output Q
 - **clock-to-Q propagation delay:**
denoted t_{pcq} , this is the maximum length of time after the clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- The inputs of a sequential circuit must be stable during the *setup* and *hold* time to guarantee that that flip-flop samples signals when they are stable
- t_{setup} , t_{hold} , t_{ccq} , and t_{pcq} are set by the manufacturer

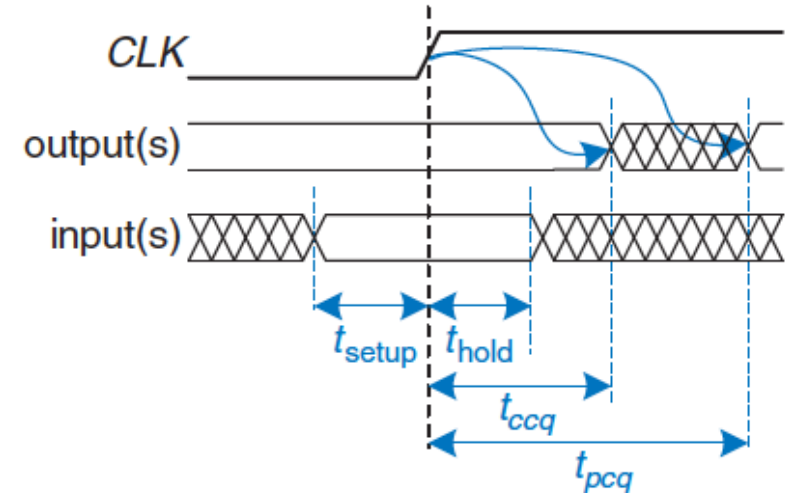


System Timing

- The clock period or cycle time, T_c , is the time between rising edges of a repetitive clock cycle.
 - Measures of time:
 - 1 millisecond (ms) = 1 thousandth second = 10^{-3} second
 - 1 microsecond (μ s) = 1 millionth second = 10^{-6} second
 - 1 nanosecond (ns) = 1 billionth second = 10^{-9} second
 - 1 picosecond (ps) = 1 trillionth second = 10^{-12} second
- Its reciprocal, $1/T_c$, is the *clock frequency*.
 - Measures of speed:
 - 1 kilohertz (KHz) = 1 thousand Hz = 10^3 Hz
 - 1 megahertz (MHz) = 1 million Hz = 10^6 Hz
 - 1 gigahertz (GHz) = 1 billion Hz = 10^9 Hz
 - 1 terahertz (THz) = 1 trillion Hz = 10^{12} Hz
- All else being same, increasing the clock frequency increases the work a digital system can accomplish per unit time.

Analyzing Timing Constraints

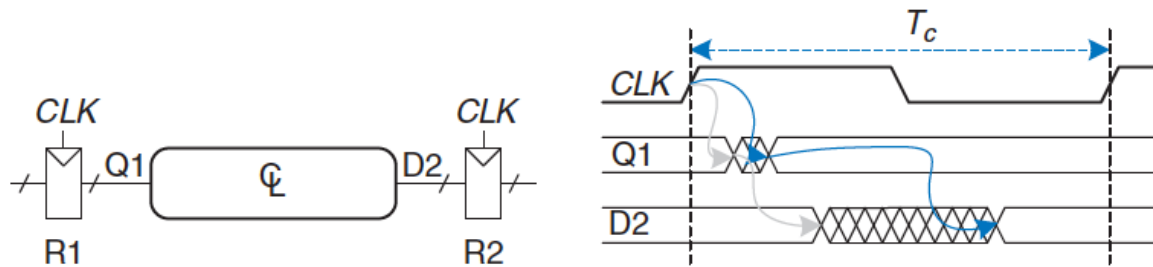
- Consider the sequential circuit below whose clock period we wish to determine



- On the rising edge of the clock, register $R1$ produces $Q1$
- $Q1$ enters a combinational logic block and produces $D2$, the input to register $R2$
- Gray arrows indicate contamination delay thru $R1$ and combinational logic
- Blue arrows indicate propagation delay thru $R1$ and combinational logic
- We will use this to analyze the setup time and hold time of $R2$


Setup Time Constraint

- D2 must settle no later than the *setup time* before the next clock edge
- Hence, the clock period cannot be shorter than the propagation delay of R1 and the combinational logic and setup time of R2
 - $T_c \geq t_{pcq} + t_{pd} + t_{setup}$
- Clock period is often set by marketing in commercial designs
- Propagation delays and setup times are set by the manufacturer of the flip-flops
- Hence, we rearrange to obtain an upper bound on t_{pd}
 - $t_{pd} \leq T_c - (t_{pcq} + t_{setup})$
- This inequality is the *setup time constraint* or *max-delay constraint*

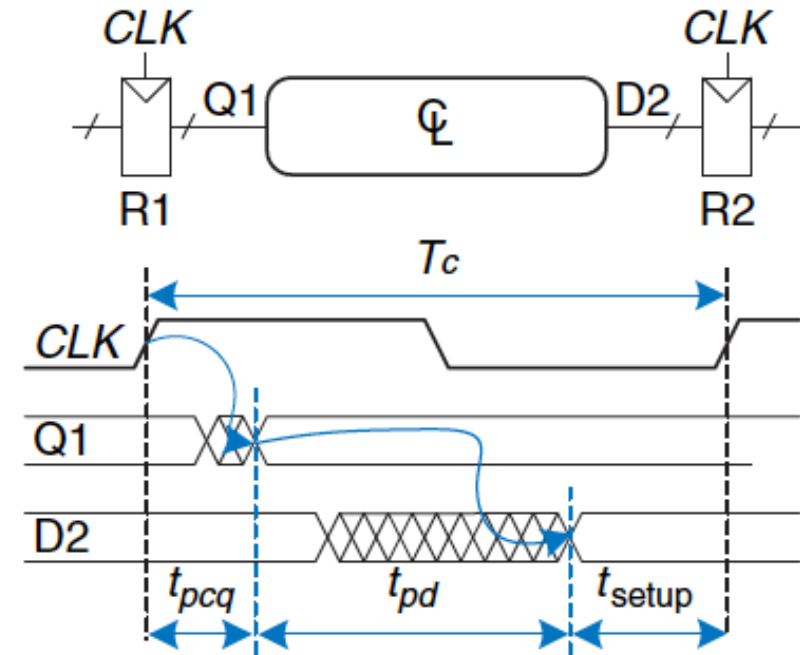


Setup Time Constraint

- The term $(t_{pcq} + t_{setup})$ is called sequencing overhead
- Ideally, the entire clock period is available to combinational logic, but sequencing the flip-flop cuts into the time
- What happens if t_{pd} is too large?
 - D2 may not have settled when R2 samples it
 - The circuit will malfunction
- To solve this problem, either
 - Increase clock period, or
 - Shorten combinational logic propagation delay

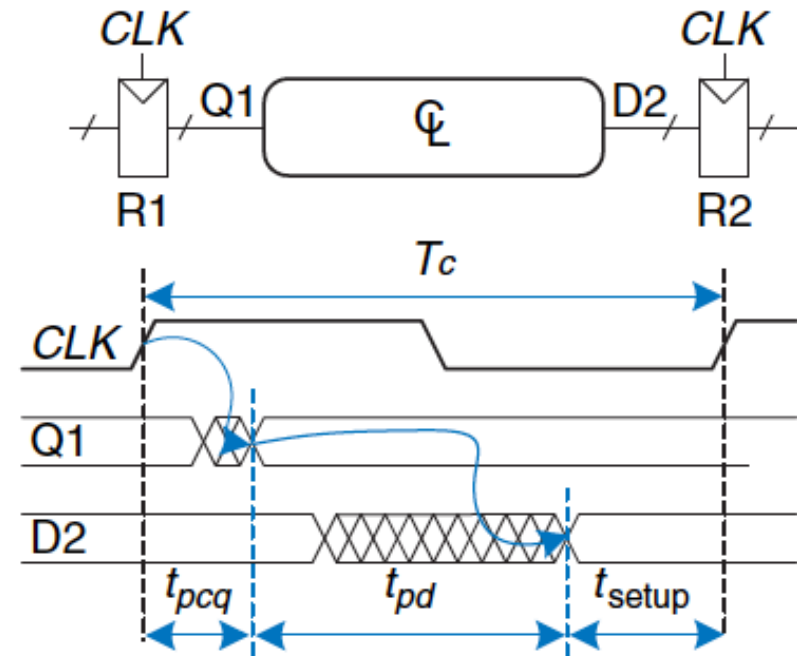


Hold Time Constraint

- Recall that the input data needs to be stable for t_{hold} time after the clock's rising edge for the circuit to sample correctly
- The register R2 must also have a *hold time constraint*
- The figure shows that D2 will change as early as $t_{ccq} + t_{cd}$ after the rising edge of the clock. Why?
 - Q1 changes as early as t_{ccq}
- Hence, it must be that $t_{hold} \leq t_{ccq} + t_{cd}$
- But t_{hold} and t_{ccq} are fixed by manufacturers
- Therefore, we rearrange the inequality to get a lower bound on t_{cd}
 - $t_{cd} \geq t_{hold} - t_{ccq}$ (hold time constraint or min-delay constraint)

 

Hold Time Constraint

- What will happen to *hold time constraint* if two flip-flops are cascaded back-to-back, with no combinational logic between them (see figure)
 - $t_{cd} = 0$. No contamination delay due combinational logic
 - Hence, hold time constraint is $t_{hold} \leq t_{ccq}$
- *Thus, a reliable flip-flop must have a hold time shorter than its contamination delay*
- Often flip-flops are designed to have $t_{hold} = 0$, hence the constraint will always hold
- Even then, hold time constraint is critical
 - If violated the only solution is to increase contamination delay or add buffers to increase delay
 - This involves redesigning the circuit, which is expensive
- In further discussions, we will assume that $t_{hold} = 0$ unless stated otherwise

 


Putting It Together

- Sequential circuits have setup and hold time constraints that dictate the max and min delays of combination circuits between flip-flops
- Modern flip-flops are designed assuming that min delay thru combinational logic is 0, i.e, flip-flops can be cascaded back-to-back
- The max delay constraint limits the no. of consecutive gates on the critical path of a circuit, because a high frequency means a shorter clock period

Timing Analysis: Example #1

 - Consider the circuit below and the given timing specifications
- Suppose we wanted to compute the minimum clock period for this circuit to function properly.



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

 - We know that $T_c \geq t_{pcq} + t_{pd} + t_{setup}$
- t_{pcq} and t_{setup} are fixed. Hence, we determine t_{pd} along critical path



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

 - The critical path occurs when A rises from 0 to 1, B = 1, C = 0, and D = 0
- 3 gates activated along critical path. Hence, $t_{pd} = 3 \times 35 = 105$ ps



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

 - Hence, $T_c \geq t_{pcq} + t_{pd} + t_{setup} \Rightarrow T_c \geq 50 + 105 + 60 = 215 \text{ ps}$
- Max. clock frequency, $1/T_c$, is approx. 4.5 GHz



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

 - Let us check the hold time constraint
- We know that $t_{hold} \leq t_{ccq} + t_{cd}$
- We need to compute t_{cd} since the others are fixed



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

 - t_{cd} dictates the earliest time when the input will begin to change after the rising edge of the clock cycle
- Hence, t_{cd} is based on the shortest path that occurs when $A = 0$ and C rises



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

 - Thus, $t_{cd} = 25 \text{ ps}$ (involves only 1 gate)
- $t_{hold} \leq t_{ccq} + t_{cd} \Rightarrow 70 \leq 55$ (constraint not met!)



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

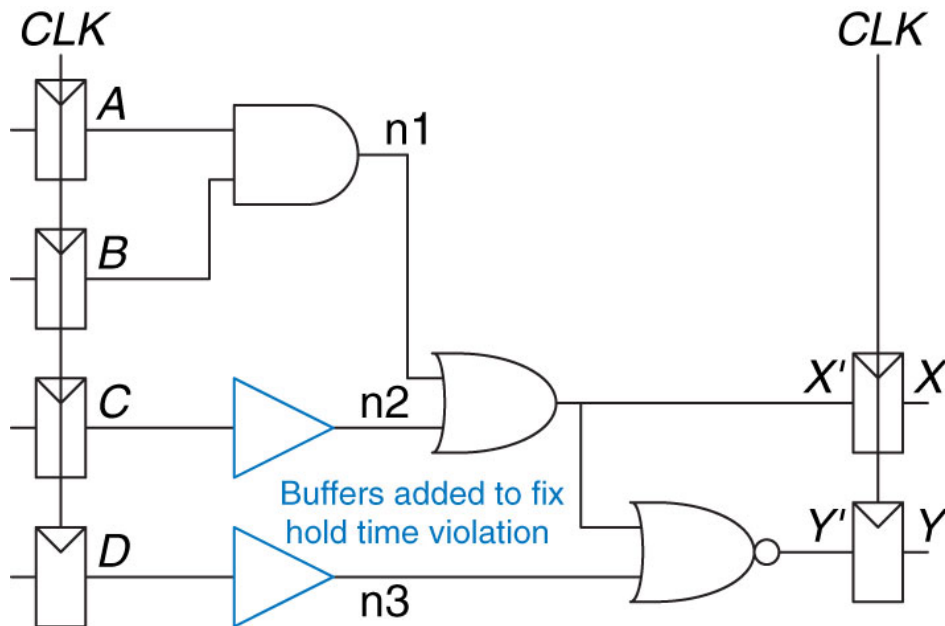- Hold time constraint violation can be fixed by increasing delay
- To this end, we add buffers after C and D. Why both C and D?
 - Because if $D = 1$, the Y' will change before X' causing the hold time constraint violation again!



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$


Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

Timing Analysis: Example #1

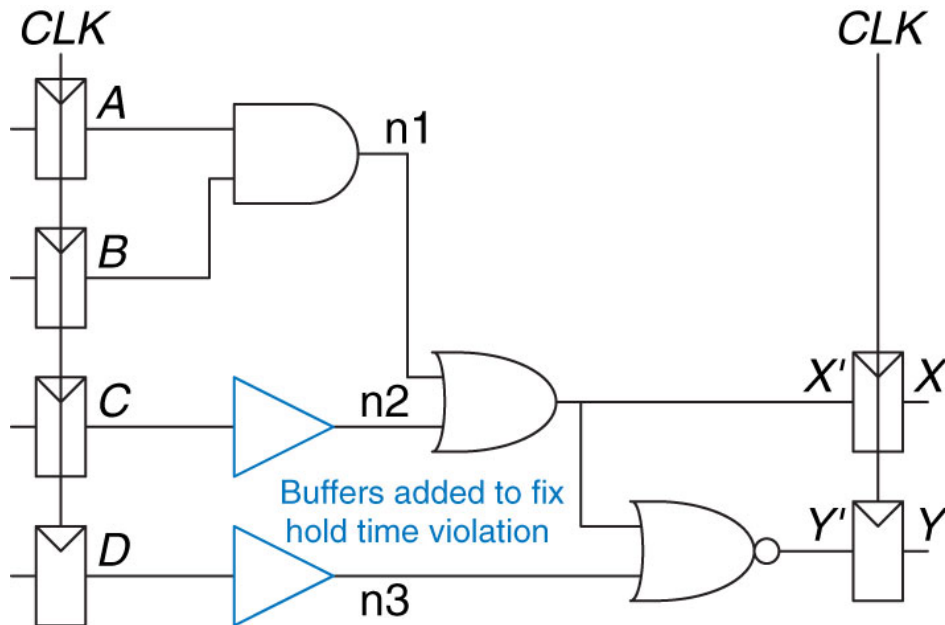- Thus, $t_{cd} = 50 \text{ ps}$ (involves 2 gates)
- $t_{hold} \leq t_{ccq} + t_{cd} \Rightarrow t_{hold} \leq 80 \text{ ps}$ (constraint met!)
- However, this will slow down the circuit



Flip-flops

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

Gates

$$t_{cd} = 25 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$