

# Unit 10: Arithmetic Logic Units

CSE 220: System Fundamentals I

Stony Brook University


Joydeep Mitra

# Arithmetic Circuits

- Arithmetic circuits are fundamental building blocks of computers
- We will look at the implementations of a few basic arithmetic functions: addition, subtraction, and comparators
- We will then see how they can be combined to a single unit called the ALU
 
# Addition

- Let's consider the simple case of adding two bits
- This can be done by a *1-bit half adder*
  - Takes two inputs, A and B
  - Produces two outputs, S and  $C_{out}$




$A$	$B$	$C_{out}$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$
$$C_{out} = AB$$

- The half adder can be built from an XOR gate and an AND gate
 
# Addition

- But what about adding more than 1 bit?
  - We need to build a multi-bit adder, where the carry out should propagate to the carry in of the next most significant bit
- This problem is solved by using the *full adder*
  - Takes three inputs,  $A$ ,  $B$ ,  $C_{in}$
  - Produces two outputs,  $S$  and  $C_{out}$
  - $C_{in}$  is  $C_{out}$  of the previous bit




$C_{in}$	$A$	$B$	$C_{out}$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

- The *full adder* can be built from 2 half adders
 
# Addition


- An adder that performs multi-bit addition is called a *Carry Propagate Adder (CPA)*. Why?
  - Since the carry out of one bit propagates into the next bit as a carry in
  - It is represented as full adder, except that  $A, B$ , and  $S$  are actually buses and not single bits



- There are many ways of implementing a CPA; we will discuss one of them, the **ripple carry adder**
 
# Ripple Carry Adder


- A ripple carry adder is implemented by chaining together N full adders, each adder feeding a carry out to the carry in of the next adder
- The carry values ripple through from the lsb to the msb



- A limitation of this implementation is that it's slow. Why?
  - $S_{31}$  depends on  $C_{30}$ , which depends on  $C_{29}$ , and so on till  $C_{in}$
  - Hence, the critical path grows with N, where N is the no. of full adders
  - Longer critical path implies longer (propagation) delays


 
# Ripple Carry Adder

- If the propagation delays of the gates in a full adder are given to us, then what will be the propagation delay of one full adder circuit? Assume time in nanoseconds.


  
# Ripple Carry Adder

- Now, imagine the delay for a ripple carry adder for 4 bit addition




- The propagation delay is 19 ns
- An alternative implementation optimizes the delay by looking ahead at certain adders and predicting their sum and carry outs.



 
# Subtraction

- Subtraction is just addition of a positive number with a negative number
- We know that the binary negative number is represented as two's complement
- So, subtracting B from A is the same as adding the two's complement of B to A
  - $A - B = A + B' + 1$




 
# Magnitude Comparison

- Comparing two numbers A and B is the same as performing subtraction and checking the sign bit. E.g.,
  - $A > B \iff 1$  if sign bit of  $A - B$  is 0; 0 if sign bit of  $A - B$  is 1
  - $A < B \iff 1$  if sign bit of  $A - B$  is 1; 0 if sign bit of  $A - B$  is 0
- Basically, the output of a magnitude comparison is the value of the sign bit or its complement; depends on your requirement specification


  
# Equality Comparison

- Equality comparison between  $A$  and  $B$  requires us to compare every bit in  $A$  and  $B$ , a bit like addition
  - $A = B$  if all bits are equal; if at least one is unequal, then  $A \neq B$
- Note that the XNOR gate can be used to identify if the two inputs are equal
- Every bit of  $A$  and  $B$  can be XNOR-ed and the output fed to an AND gate



# Building An ALU

- Until now, we have seen individual operations
- Building an ALU involves combining numerous operations (arithmetic and logical) into one unit
- General Idea:
  - Every operation in an ALU is identified by an **opcode**
  - A multiplexer is used to select between the different opcodes
  - Each operation is implemented by building an ALU for each bit of the operands in the operation
    - For N-bit operands, we will have N ALUs chained together; the output of 1 ALU may be the input of another ALU

# Example #1

- Consider the set of operations/functions in the table for which we will build an ALU
- $F_{2:0}$  is a 3-bit signal, which indicates the opcode for each operation
  - E.g., 000 indicates the ALU output should be  $A \text{ AND } B$
- Assume we have an N-bit adder, a two input AND gate and OR gate, and a NOT gate. We also have a 2:1 MUX and a 4:1 MUX

$F_{2:0}$	Function
000	$A \text{ AND } B$
001	$A \text{ OR } B$
010	$A + B$
011	not used
100	$A \text{ AND } \bar{B}$
101	$A \text{ OR } \bar{B}$
110	$A - B$
111	SLT

# Example #1


- We see that few operations need an adder, which needs an input  $C_{in}$
- We also observe that the operations are similar (with difference in operands) when  $F_2 = 0$  and  $F_2 = 1$
- We re-arrange the table according to our observations

$F_2$	$F_{1:0}$	Function	$C_{in}(\text{Bit } 0)$
0	00	A AND B	X
0	01	A OR B	X
0	10	A + B	0
0	11	Not used	X

$F_2$	$F_{1:0}$	Function	$C_{in}(\text{Bit } 0)$
1	00	A AND B'	X
1	01	A OR B'	X
1	10	A - B (A+B'+1)	1
1	11	SLT (A+B'+1)	1
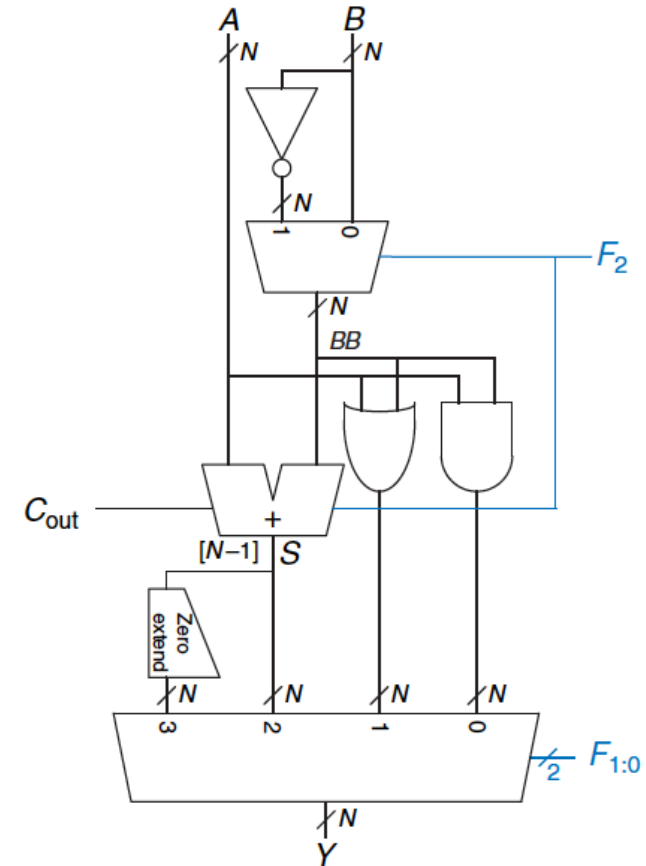
# Example #1

- We use the 4:1 MUX with  $F_{1:0}$  control signals to select between the functions -- AND, OR, +, -
- We use the 2:1 MUX with  $F_2$  to select between B and B'
- Note that  $F_2$  and  $C_{in}$  have the same values
- For the SLT function, we just need the *msb* of  $A+B+1$  as the *zero-extended* output



# ALU Flags

- Some ALUs produce extra outputs, called *flags*
- *Flags* indicate additional information about the output. E,g,.
  - An *overflow* flag that result has overflowed
  - A *zero* flag indicates that the output is 0
- The additional information from flags can be used to makes decisions about the final output or to select certain inputs for the next ALUs in the circuit



# Example #2

- Design a 3-bit ALU for the following functions:
  - We can only use 8:1 MUX, 2:1 MUX, half adders, and NOT gates inside an ALU

C2 C1 C0	Function
0 0 0	A XOR B
0 0 1	A AND B
0 1 0	A + B
0 1 1	A NAND B
1 0 0	SGTE (Set to 1 if A >= B)
1 0 1	SLT (Set to 1 if A < B)
1 1 0	A - B
1 1 1	A NOR B

# Example #2

- First reason about the operands
  - Specifically, whether function operands need to be  $A, B, A'$ , or  $B'$
- Next, reason how to express each function with the available hardware

C2 C1 C0	Function	Translated Function
0 0 0	A XOR B	Sum output of half adder ( $A + B$ )
0 0 1	A AND B	Carry out of half adder ( $A + B$ )
0 1 0	$A + B$	Sum of full adder ( $A+B$ ; Carry out is Carry in of next bit)
0 1 1	A NAND B	$(A \text{ AND } B) \text{ XOR } 1$
1 0 0	SGTE (Set to 1 if $A \geq B$ )	NOT SLT
1 0 1	SLT (Set to 1 if $A < B$ )	$A + B' + 1$ (consider only MSB)
1 1 0	$A - B$	$A + B' + 1$
1 1 1	A NOR B	$A'B'$ (Carry out of half adder)

## Example #2





- We need control/select signals to select between operands that use the same hardware
  - Ainv** selects between A and A'
  - Binv** selects between B and B'
  - K** selects the input for the 2<sup>nd</sup> half adder
  - Less** selects between SGTE and SLT

C2 C1 C0	Function	Ainv	Binv	K	Less	Cin (LSB)
0 0 0	A XOR B	0	0	X	X	X
0 0 1	A AND B	0	0	X	X	X
0 1 0	A + B	0	0	0	X	0
0 1 1	A NAND B	0	0	1	X	X
1 0 0	SGTE (Set to 1 if A >= B)	0	1	0	0	1
1 0 1	SLT (Set to 1 if A < B)	0	1	0	1	1
1 1 0	A - B	0	1	0	X	1
1 1 1	A NOR B	1	1	X	X	X

$$\begin{aligned}
 \text{Ainv} &= C_2 C_1 C_0 & \text{Binv} &= C_2 \\
 \text{K} &= C_1 C_0 & \text{Less} &= C_0 \\
 \text{Cin (LSB)} &= C_2
 \end{aligned}$$


# Example #2

Available Hardware

    


## Example #2

- LSB ALU

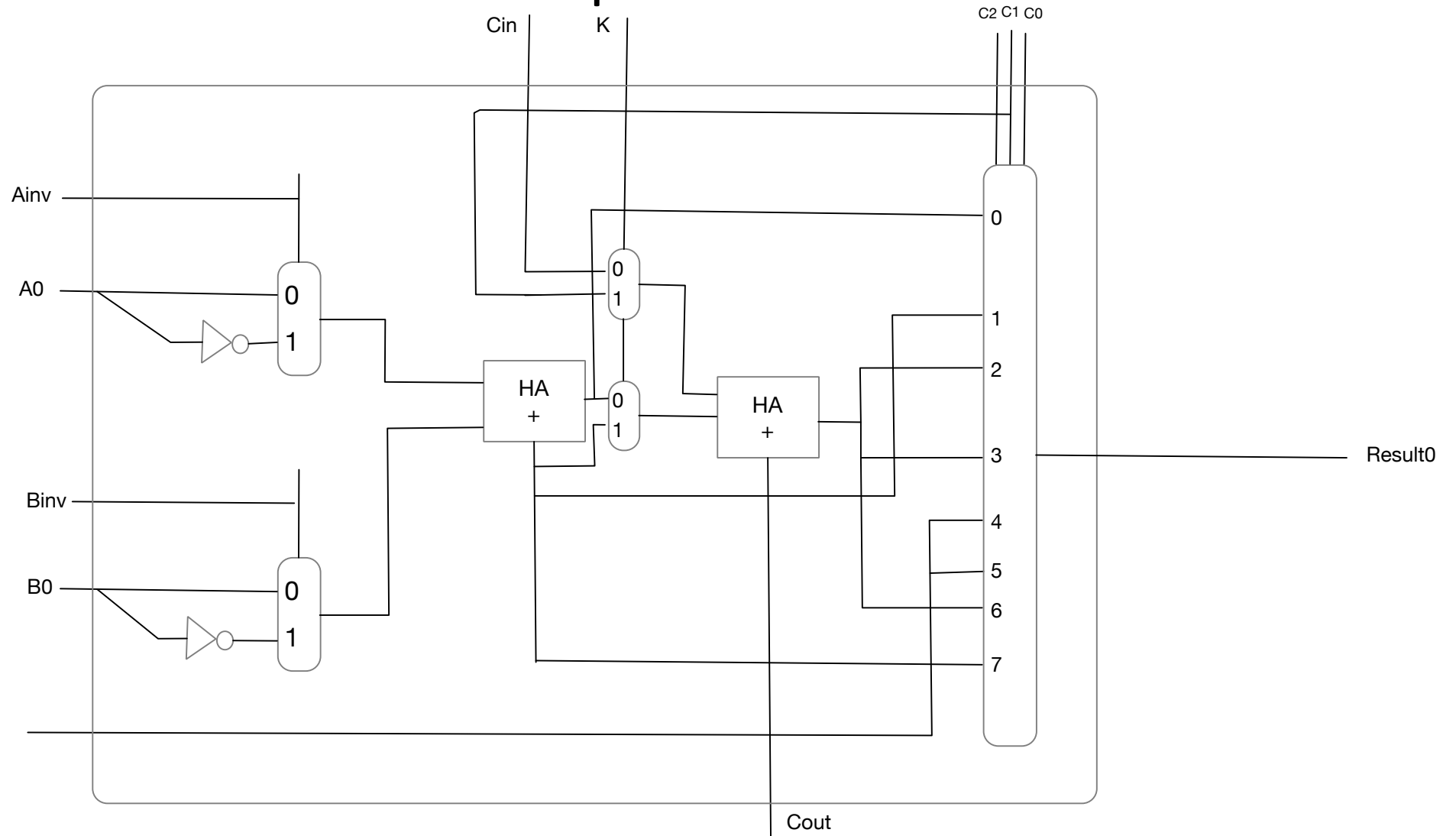

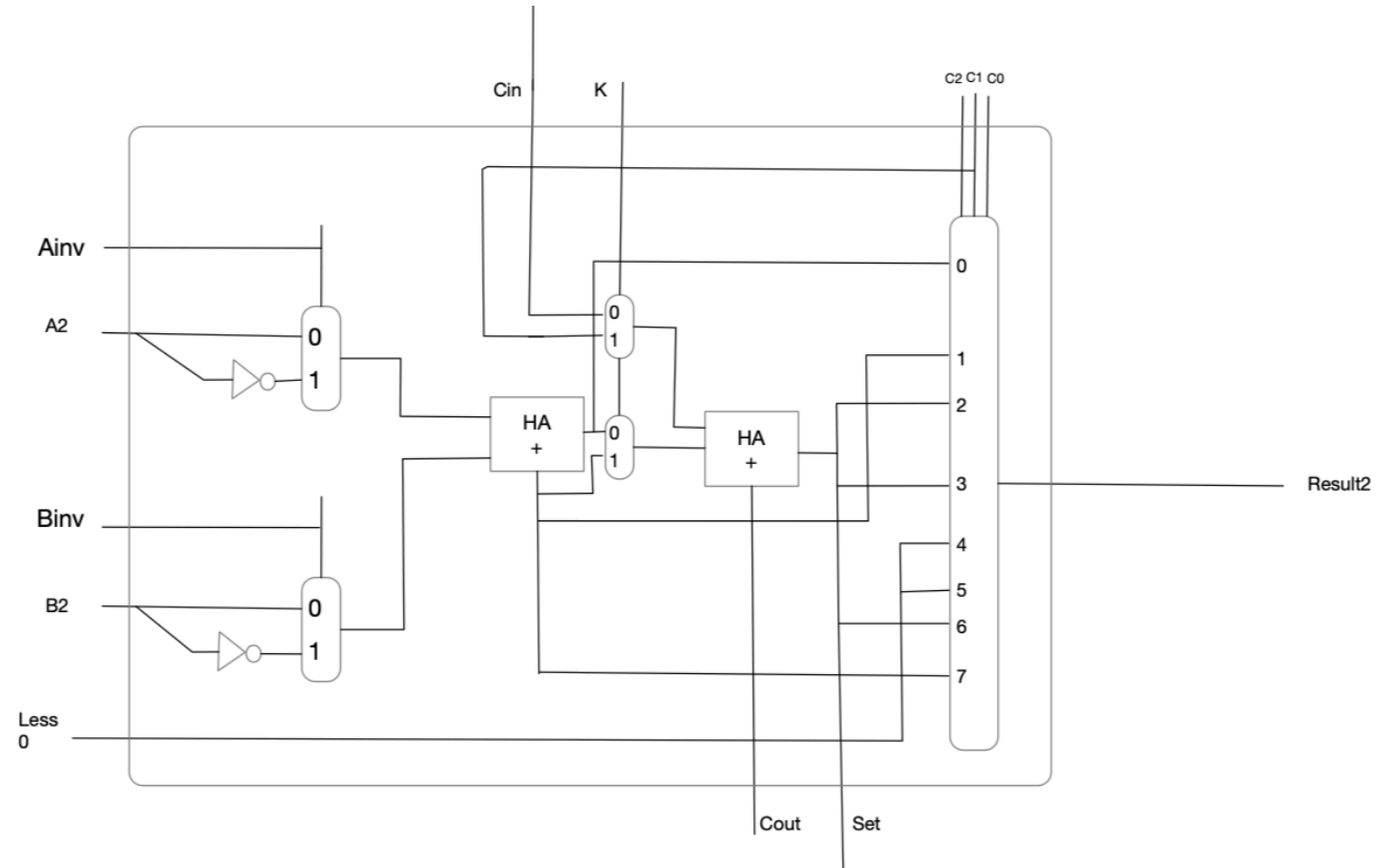
# Example #2

- The MSB will be the same as LSB except we will have to wire the comparator functions appropriately



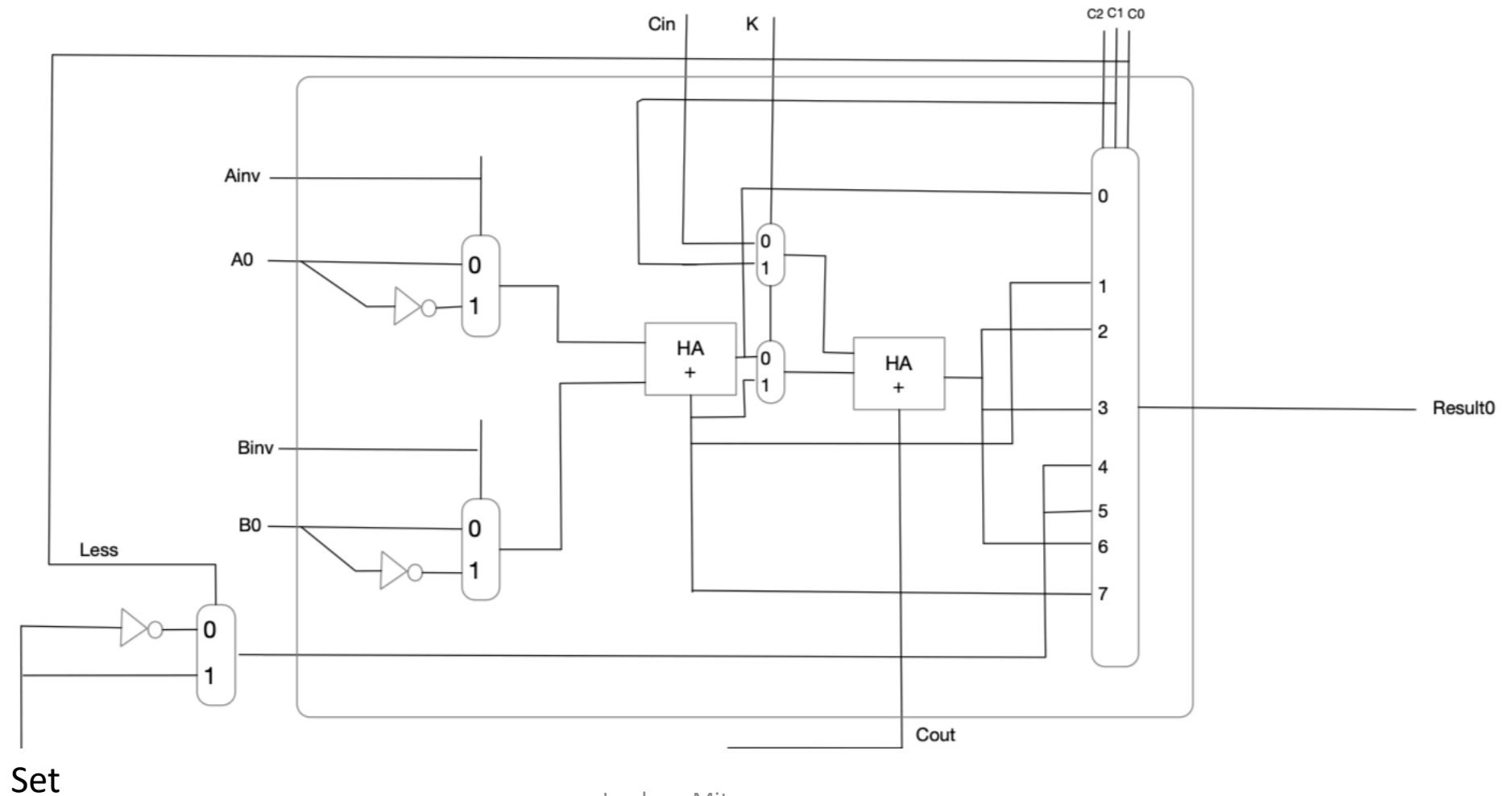
# Example #2

- The LSB ALU needs to be modified to account for the Set bit from MSB



# Example #2

- A snapshot of the 3-bit ALU

 



# ALU Recap

- Arithmetic circuits are fundamental building blocks of computers
- We have seen implementations of a few basic arithmetic functions: addition, subtraction, and comparators
- We have seen examples of how ALUs can be used to implement a multitude of operations

# Example #3


- Design the LSB and MSB ALU for the following functions

C2 C1 C0	Function
0 0 0	A + B
0 0 1	A NOR B
0 1 0	SGT (A > B)
0 1 1	unused
1 0 0	A AND B
1 0 1	A XOR B
1 1 0	A - B
1 1 1	Set Even ( A is even)

# Example #3

## Available Hardware

- we can add at most one 2:1 MUX

 

# Example #3

- Express the functions in available hardware

C2 C1 C0	Function	Translated Function
0 0 0	A + B	Full Adder with A, B, Cin (Sum)
0 0 1	A NOR B	Full Adder with A', B', Cin = 0 (Carry out)
0 1 0	SGT (A > B)	Full Adder with A', B, Cin = 1 (MSB of Sum)
0 1 1	unused	Ground
1 0 0	A AND B	Full Adder with A, B, Cin = 0 (Carry out)
1 0 1	A XOR B	Full Adder with A, B, Cin = 0 (Sum)
1 1 0	A - B	Full Adder with A, B, Cin = 1 (Sum)
1 1 1	Set Even ( A is even)	LSB of A'

# Example #3

- We need the following control/select signals to select between operands that use the same hardware
  - **Ainv** to select between A and A'
  - **Binv** to select between B and B'
  - **S** to select between arithmetic and logical functions

C2 C1 C0	Function	Ainv	Binv	S	Cin (LSB)
0 0 0	A + B	0	0	0	0
0 0 1	A NOR B	1	1	1	0
0 1 0	SGT (A > B)	1	0	0	1
0 1 1	unused	X	X	X	X
1 0 0	A AND B	0	0	1	0
1 0 1	A XOR B	0	0	1	0
1 1 0	A - B	0	1	0	1
1 1 1	Set Even (A is even)	1	X	X	X


$$\mathbf{Ainv} = C_2' (C_0 + C_1) + C_1 C_0$$

$$\mathbf{Binv} = C_2' C_0 + C_2 C_1$$

$$\mathbf{S} = C_2 C_1' + C_0$$

$$\mathbf{Cin} = C_1$$

# Example #3

 


C2 C1 C0	Function	Ainv	Binv	S	Cin
0 0 0	A + B	0	0	0	0
0 0 1	A NOR B	1	1	1	0
0 1 0	SGT (A > B)	1	0	0	1
0 1 1	unused	X	X	X	X
1 0 0	A AND B	0	0	1	0
1 0 1	A XOR B	0	0	1	0
1 1 0	A - B	0	1	0	1
1 1 1	Set Even (A is even)	1	X	X	X

## The LSB ALU


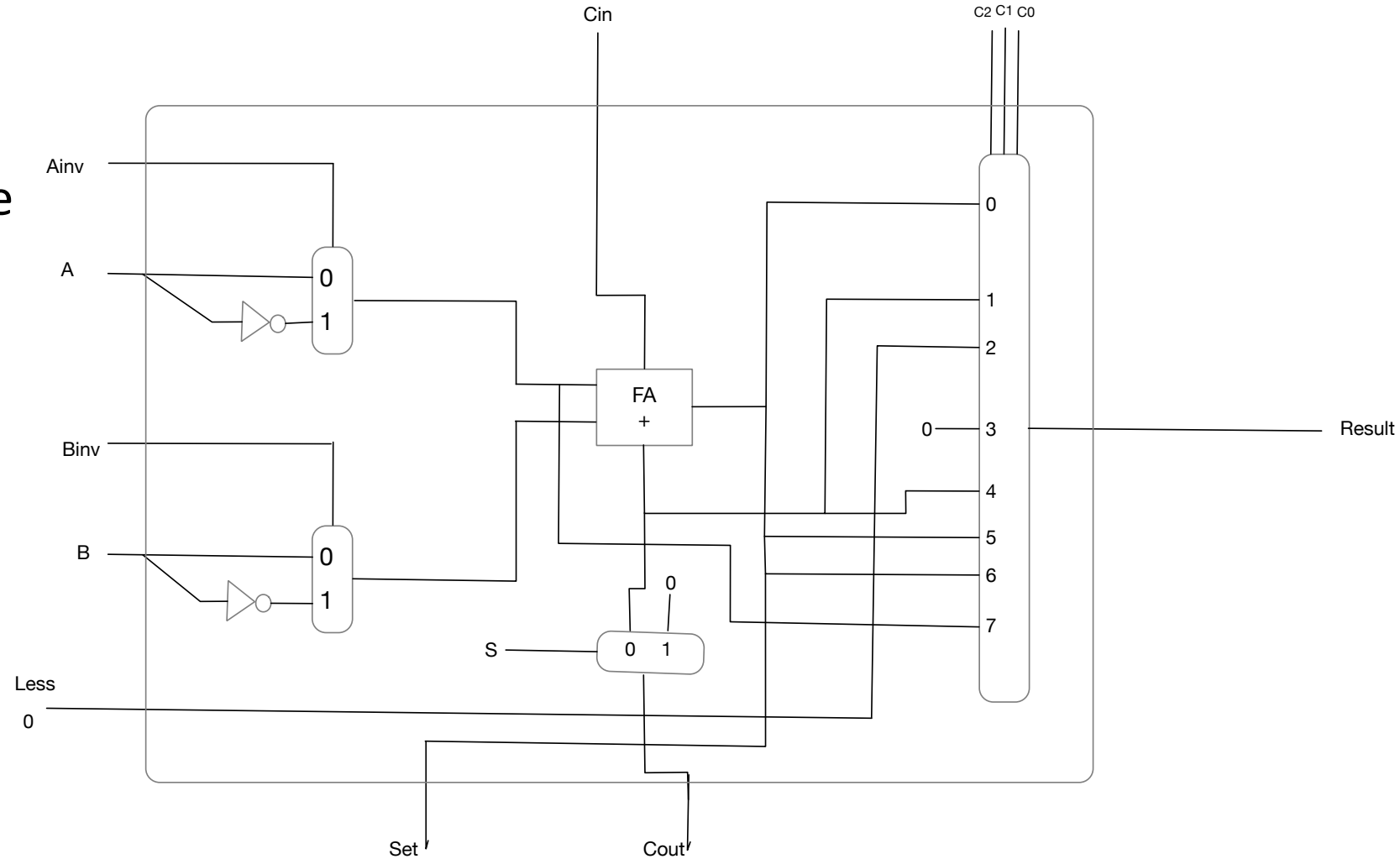
# Example #3

- The MSB ALU is the same as LSB except the **Set** signal is connected to the Sum output of the full adder
- The Set output is connected back to the LSB **Less** signal
- The MSB **Less** signal is 0






# Example #4

- Design a 3-bit ALU for the following functions

C2 C1 C0	Function
0 0 0	SEQ (A = B)
0 0 1	A NOR B
0 1 0	A OR B
0 1 1	A AND B
1 0 0	A - B
1 0 1	A + B
1 1 0	A XOR B
1 1 1	2A

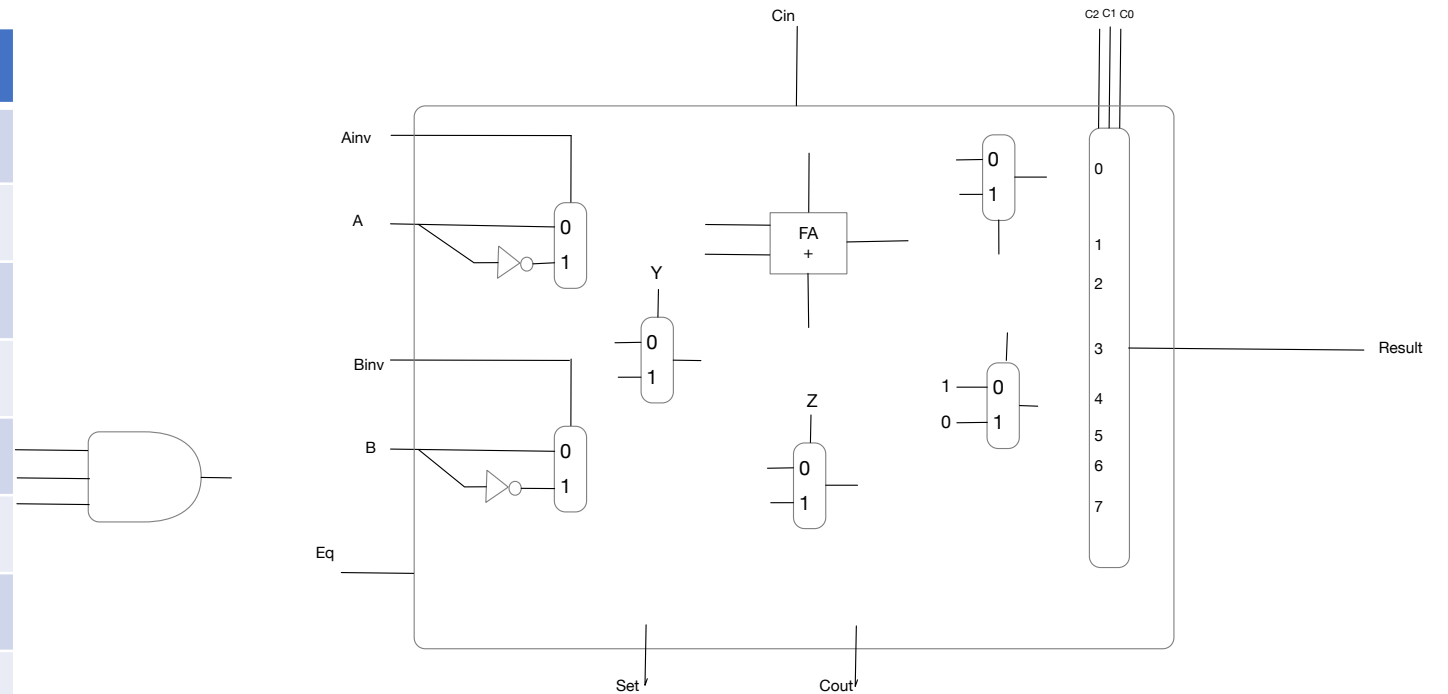

## Available Hardware

# Example #4

- Boolean Equations for Control/Select signals


$C_2 C_1 C_0$	Function	$A_{inv}$	$B_{inv}$	Y	Z	$C_{in}(LSB)$
0 0 0	SEQ (A = B)	0	0	0	1	0
0 0 1	A NOR B	1	1	0	1	0
0 1 0	A OR B	1	1	0	1	0
0 1 1	A AND B	0	0	0	1	0
1 0 0	A - B	0	1	0	0	1
1 0 1	A + B	0	0	0	0	0
1 1 0	A XOR B	0	0	0	1	0
1 1 1	2A	0	X	1	0	0

$$\begin{aligned}
 A_{inv} &= C_2' (C_1 \text{ XOR } C_0) \\
 B_{inv} &= C_2' (C_1 \text{ XOR } C_0) + C_2 C_1' C_0' \\
 Y &= C_2 C_1 C_0 \\
 Z &= C_2' + C_1 C_0' \\
 C_{in} &= C_2 C_1' C_0'
 \end{aligned}$$

- Y is used to select between A and B
- Z is used to select between arithmetic and logical operations

# Example #4

- Available Hardware

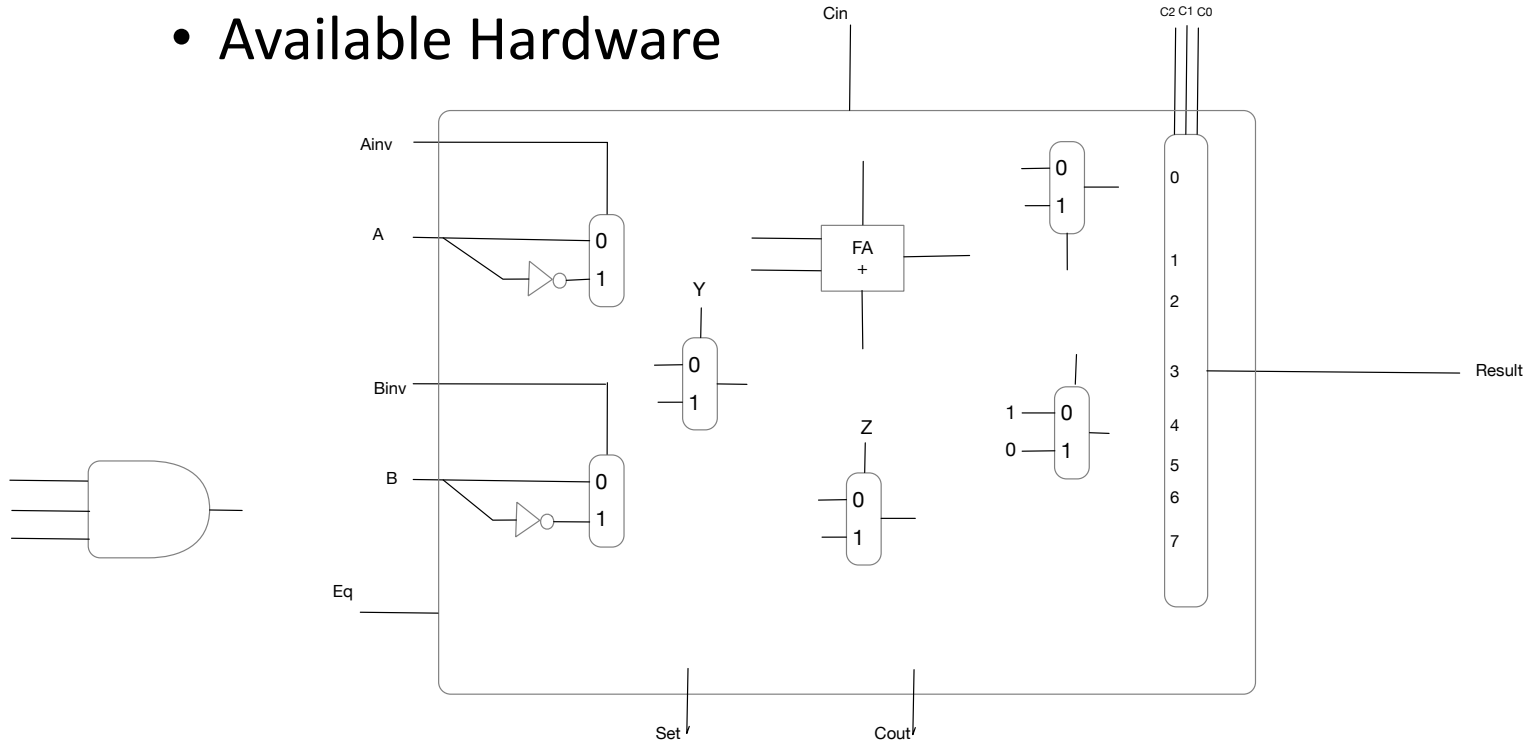

C2 C1 C0	Function	Ainv	Binv	Y	Z	Cin
0 0 0	SEQ (A = B)	0	0	0	1	0
0 0 1	A NOR B	1	1	0	1	0
0 1 0	A OR B	1	1	0	1	0
0 1 1	A AND B	0	0	0	1	0
1 0 0	A - B	0	1	0	0	1
1 0 1	A + B	0	0	0	0	0
1 1 0	A XOR B	0	0	0	1	0
1 1 1	2A	0	X	1	0	0

## Example #4

- LSB ALU
- The middle bit ALU and MSB ALU are the same as the LSB ALU

